



DON BOSCO COLLEGE

(Affiliated to the University of Calicut)

Mannuthy, Thrissur 680 651, Tel: 0487 - 2373730, 2371337, 2370447

E-mail: dbciqacmty@gmail.com , dbctrichur@gmail.com, iqac@dbcollegemannuthy.edu.in

www.dbcollegemannuthy.edu.in,

SECOND INTERNAL EXAMINATION OCTOBER 2015

THIRD SEMESTER B.Sc. CS

BCS3B04 – FUNDAMENTALS OF DIGITAL ELECTRONICS

Time : 3 hours

Total Marks :80

Part- A

Answer all questions

(Each carries 1 mark)

1. The number 10 in Hexadecimal system is equivalent to ----- in decimal system.
2. Hamming distance between 1001 and 10110 -----
3. A quad in a K-Map can eliminate ----- variables from a Boolean expression.
4. The complemented OR gate is called a-----
5. $A + B =$
6. The IC 7483 is a-----
(a)BCD Adder (b)comparator (c)multiplexer
(d)demultiplexer
7. The sum of the half adder is-----
8. Single input version of J-K flip –flop formed by tying both the inputs of j-k is -

9. Memory is a circuit ,which is used to store ----information
(a)Accurate (b)Discrete (c)Analog (d)Digital
10. A register is a rroup of -----suitable for storing binary information.

(1*10=10 marks)

Part -B

Answer any five

(Each carries 2 marks)

1. What is SR flip flop?
2. What is a sequential logic circuit?
3. Write a note on Decoder.
4. State the De Morgan's law
5. What is parity bit? Explain its use?



DON BOSCO COLLEGE

(Affiliated to the University of Calicut)

Mannuthy, Thrissur 680 651, Tel: 0487 - 2373730, 2371337, 2370447

E-mail: dbcqacmty@gmail.com, dbctrichur@gmail.com, iqac@dbccollegemannuthy.edu.in

www.dbcollegemannuthy.edu.in,

6. Convert the binary number 101010.01 into decimal.
7. Prove $AC+ABC=C(A+B)$.
8. Write the symbols used in a number system with base 16

(2*5=10 marks)

Part -C

Answer any five

(Each carries 4 marks)

1. What is a full-adder? Obtain its truth table.
2. Explain the behavior of JK flip-flop.
3. Design a half subtractor with basic gates.
4. What is a binary parallel adder?
5. What is a decoder? Explain the functioning of a basic binary decoder?
6. Describe different types of shift registers.
7. Convert following binary to hexadecimal:

(a) 110011.11

(b) 1111000.101

(4*5=20 marks)

Part -D

Answer any five

(Each carries 8 marks)

1. Discuss any three number systems along with rules for converting from one number system to another. Illustrate with examples.
2. What are magnitude comparators? Explain the design of a 4-bit magnitude comparator.
3. What is an encoder? Explain the design of octal-to-binary-encoder.
4. Describe different types of computer codes.
5. Obtain the simplified expression for the Boolean function $AC+BC+BC+ABC$ in standard SOP form. Draw the gate implementation of simplified function using AND and OR gates.



DON BOSCO COLLEGE

(Affiliated to the University of Calicut)

Mannuthy, Thrissur 680 651, Tel: 0487 - 2373730, 2371337, 2370447

E-mail: dbcqacmty@gmail.com , dbctrichur@gmail.com, iqac@dbcollegemannuthy.edu.in

www.dbcollegemannuthy.edu.in,

6. What is a multiplexer? Design a 8X1 multiplexer.
7. What is a JK flip-flop? Draw its circuit diagram. Obtain its characteristic table and characteristic equation .Explain its behavior using its timing diagram.

(8 *5=40 marks)
